Digital Design and Computer Organization Assignment 2 UE21CS251A

3rd Semester, Academic Year 2021-22

ASSIGNMENT 2

Name: SRN: PES1UG21CS367 Section: F

FLIPFLOPS

1. SR FlipFlop

Code:

Module file:

```
module srf(input wire clk,s,r,output wire q,q_b);
reg s_o,r_o;
always @(posedge clk) begin
s_o <= !(s & clk);
r_o <= !(r & clk);
end
nand2 nand2_3(s_o,q_b,q);
nand2 nand2_4(r_o,q,q_b);
endmodule
```

Testbench:

`timescale 1 ns/100 ps

```
module tb;
reg t_s,t_r,clk;
wire t_q,t_q_b;
reg [1:0] i_p [0:4];
integer i;
initial begin
$dumpfile("dumpSR.vcd");
$dumpvars(0,tb);
end
initial clk=1'b0; always #5 clk =~clk;
initial begin
i_p[0][1:0]=2'b01;
i_p[1][1:0]=2'b00;
i_p[2][1:0]=2'b01;
i_p[3][1:0]=2'b10;
i_p[4][1:0]=2'b11;
end
initial {t_s,t_r, i} =0;
srf srf_1(clk,t_s,t_r,t_q,t_q_b);
initial begin
#5
for(i=0;i<5;i=i+1)
begin
#10 {t_s,t_r}=i_p[i];
end
#30
$finish;
```

endmodule

Compiling files:

```
SC:\iverilog\bin>iverilog -o xyz lib.v srtb.v sr.v

C:\iverilog\bin>vvp xyz

VCD info: dumpfile dumpSR.vcd opened for output.

C:\iverilog\bin>gtkwave dumpSR.vcd


GTKWave Analyzer v3.3.48 (w)1999-2013 BSI

[0] start time.

[85000] end time.

WM Destroy
```

OUTPUT WAVEFORM:

 

2. JK FlipFlop

Code:

Module file:

```
module jkf(input wire clk,reset,j,k,output wire q,q_b);
reg s_in,r_in,q_out,q_b_out;
wire s_in_w,r_in_w;
reg a_s_o,a_r_o;
always @(posedge clk,posedge reset) begin
if(reset == 0) begin
if(k == 0 \& j == 0) begin
q_out <= q_out;
q_b_out <= q_b_out;
end
else if(k == 1 \& j == 1) begin
q_out <= ~q_out;
q_b_out <= ~q_b_out;</pre>
end
else if(j == 1) begin
q_out <= 1;
q_b_out <= 0;
end
else if(k == 1) begin
q_out <= 0;
q_b_out <= 1;
end
end
```

```
else begin
q out <= 0;
q_b_out <= 1;
end
end
assign q = q_out;
assign q_b = q_b_out;
endmodule
Testbench:
`timescale 1 ns/100 ps
module tb;
reg t_j,t_k,t_reset,clk;
wire t_q,t_q_b;
reg [2:0] i_p [0:4];
integer i;
initial begin
$dumpfile("dumpJK_FF.vcd");
$dumpvars(0,tb);
end
initial clk=1'b0; always #5 clk =~clk;
initial begin
i_p[0][2:0]=3'b101;
i_p[1][2:0]=3'b000;
i_p[2][2:0]=3'b001;
i_p[3][2:0]=3'b010;
i_p[4][2:0]=3'b011;
end
```

```
initial {t_reset,t_j,t_k,i} =0;

jkf jkf_1(clk,t_reset,t_j,t_k,t_q,t_q_b);

initial begin

#5 for(i=0;i<5;i=i+1)

begin #10 {t_reset,t_j,t_k}=i_p[i]; end

#40 $finish;

end

endmodule</pre>
```

Compiling files:

```
C:\iverilog\bin>iverilog -o xyz lib.v jktb.v jk.v

C:\iverilog\bin>vvp xyz

VCD info: dumpfile dumpJK_FF.vcd opened for output.


C:\iverilog\bin>gtkwave dumpJK_FF.vcd

GTKWave Analyzer v3.3.48 (w)1999-2013 BSI

[0] start time.
[95000] end time.

WM Destroy
```

OUTPUT WAVEFORM:

 

3.T FlipFlop

Code:

```
Module file:
module tf(input wire clk,reset,t,output wire q,q_b);
reg q_out,q_b_out;
always @(posedge clk,posedge reset) begin
if(reset == 0) begin
if(t==0) begin
q_out <= q_out;
q_b_out <= q_b_out;
end
if(t==1) begin
q_out <= ~q_out;
q_b_out <= ~q_b_out;
end
end
else begin
q_out <= 0;
q_b_out <= 1;
end
end
assign q =q_out;
assign q_b = q_b_out;
endmodule
```

Testbench:

`timescale 1 ns/100 ps

```
module tb;
reg t_tin,t_reset,clk;
wire t_q,t_q_b;
reg [1:0] i_p [0:2];
integer i;
initial begin
$dumpfile("dumpT_FF.vcd");
$dumpvars(0,tb);
end
initial clk=1'b0; always #5 clk =~clk;
initial begin
i_p[0]=2'b11;
i_p[1]=2'b00;
i_p[2]=2'b01;
end
initial {t reset,t tin,i} =0;
tf tf_1(clk,t_reset,t_tin,t_q,t_q_b);
initial begin
#10 for(i=0;i<3;i=i+1)
begin #10 {t_reset,t_tin}=i_p[i]; end
#40 $finish;
end
endmodule
```

Compiling files:

```
C:\iverilog\bin>iverilog -o xyz lib.v tff.v tfftb.v

C:\iverilog\bin>vvp xyz

VCD info: dumpfile dumpT_FF.vcd opened for output.

C:\iverilog\bin>gtkwave dumpT_FF.vcd

GTKWave Analyzer v3.3.48 (w)1999-2013 BSI

[0] start time.
[80000] end time.

WM Destroy
```

OUTPUT WAVEFORM:

